

Electronics (EC) Exam Sample Model Question Paper:

1. A series RLC circuit resonates at 1000 kHz. At frequency of 995 kHz, the circuit impedance is

- a) Resistive
- b) minimum
- c) Inductive
- d) capacitive

2. if each stage had gain of 10dB and noise figure of 10dB, then the overall noise figure of two-stage cascade amplifier will be

- a) 10
- b) 1.09
- c) 1.0
- d) 10.9

3. In Sigma delta ADC, high bit accuracy is achieved by

- a) Over sampling and noise shaping
- b) Over sampling
- c) Under sampling
- d) None of the above

4. A particular current is made up of two components: a) DC and a sinusoidal current of peak value of 1.414 A. The average value of the resultant current is

- a) Zero
- b) 24.14A
- c) 10A
- d) 14.14A

5. By doubling the sampling frequency

- a) Quantisation noise decreases by 3dB
- b) Quantisation noise density decreases by 3dB
- c) Quantisation noise increases by 3dB
- d) Quantisation noise density increases by 3dB

6. A Pulse train with a frequency of 1MHz is counted using a modulo 1024 ripple-counter built with J-K flip-flops. For proper operation of the counter the maximum permissible propagation delay per Flip Flop stage

- a) 100 n sec
- b) 50 n sec
- c) 20 n sec
- d) 10 n sec

7. The A/D converter used in a digital voltmeter could be (1) successive approximation type (2) Flash converter type (3) Dual slope converter type. The correct sequence in the increasing order of their conversion times is

- a) 1,2,3
- b) 2,1,3
- c) 3,2,1
- d) 3,1,2

8. The resolution of a D/A Converter is approximately 0.1% range. It is

- a) An 8-bit converter
- b) A 10-bit converter
- c) A 12 bit converter
- d) A 16 bit converter

9. In a microprocessor the register which holds the address of the next instruction to be fetched is

- a) Accumulator
- b) Program counter
- c) Stack pointer
- d) Instruction register

10. In microcomputer WAIT states are used to

- a) Make the processor wait during a DMA operation
- b) Make the processor wait during a power interrupt processing
- c) Make the processor wait during a power shutdown
- d) Interface slow peripherals to the processor

11. A 4-bit synchronous counter uses flip-flops with propagation delay time of 25 ns each. The maximum possible time required for change of state will be

- a) 25 ns
- b) 50 ns
- c) 75 ns
- d) 100 ns

12. An electromagnetic wave incident on a perfect conductor is:

- a) Entirely reflected
- b) Fully transmitted
- c) Partially transmitted
- d) None of these

13. Maximum coding gain in

- a) Block Codes
- b) Codes
- c) Turbo Codes
- d) RS Codes

14. Noise figure of an amplifier depends on

- a) Bandwidth
- b) Output power
- c) Power input
- d) None of the above

15. BCH code belongs to

- a) Block Codes
- b) Codes
- c) Turbo Codes
- d) None of the above

16. When a carrier is phase modulated, with an integrated modulating signal, the resultant is

- a) Phase modulated signal
- b) Frequency modulated signal
- c) Amplitude modulated signal
- d) QPSK modulated signal

17. A satellite orbiting in 600 km orbit transmits 5 GHz frequency. The Doppler shift observed at the ground station, when the satellite is over head of the station is

- a) Zero
- b) Maximum
- c) Infinity
- d) None of these

18. A communication channel disturbed by additive white Gaussian noise has a bandwidth of 4kHz and SNR of 15. The highest transmission rate that such a channel can support (in k-bits/sec) is

- a)16
- b)1.6
- c)3.2
- d)60

19. An inductor supplied with 50 V ac with a frequency of 10 kHz passes a current of 7.96 mA. The value of inductor is

- a) 1mH
- b) 10mH
- c) 100mH
- d) 1H

20. In a capacitor, the electric charge is stored in

- a) Dielectric
- b) Metal plates
- c) Dielectric as well as metal plates
- d) Neither dielectric nor metal plates

21. Oscillator requires

- a) No feedback
- b) Negative feedback
- c) Positive feedback
- d) Either positive or negative

22. Which loss in a transformer varies significantly with load?

- a) Hysteresis loss
- b) Eddy current loss
- c) Copper loss
- d) Core loss

23. When L is doubled and C is halved, the resonance frequency of series tuned circuit becomes

- a) Doubled
- b) Halved
- c) One quarter
- d) Unchanged

24. In a Series resonant circuit, with the increase in L
- a) Resonant frequency will decrease
  - b) Bandwidth will decrease
  - c) Q will increase
  - d) AN of these